

Physics 262

Practice Midterm Exam

Remember to show your work.

The real exam will be similar in form, but somewhat shorter.
You may bring a $4'' \times 6''$ notecard. You may use a calculator
for arithmetic computations.

Name: _____

Reference Material

Ph262
 Multi-stage filter parameters, based on H&H 2ed. (with 1 tiny correction), and Q values calculated to provide a more general prescription.
 For implementation with Sallen-Key or other 2-pole stages. The transfer function for each stage is:

$$G = \frac{k}{1 + \frac{j}{Q} \frac{\omega}{\omega_0} - \left(\frac{\omega}{\omega_0} \right)^2} = \frac{k}{1 + \frac{j}{Q} \frac{f}{f_0} - \left(\frac{f}{f_0} \right)^2}$$

The above is for low pass. For high pass, multiply by $(ff/f0)^2$.

Gain for a Sallen-Key stage, with equal component values, to attain the desired Q for the stage.

Quality factor, for the denominator of the response function, inferred from H&H K values.


Low pass frequency conversion factor: $\omega_0 = f_n * \omega_c / 2\pi$, where f_n or ω_c is the desired critical frequency.


These values are for low pass filters. Use $1/f_n$ for high pass!

Note that critical frequency for Butterworth and Bessel are at -3dB compared to DC, whereas for Chebyshev it's when the response leaves the specified passband ripple.

| #poles | Butterworth (flat response in passband) | | | Bessel (flat time delay in passband) | | | Chebyshev, 0.5dB ripple (sharp roll-off) | | | Chebyshev, 2dB ripple (sharp roll-off) | | |
|--------|---|----------------------------------|----------------------------------|--------------------------------------|----------------------------------|----------------------------------|--|-----------------------------------|----------------------------------|--|-----------------------------------|----------------------------------|
| | K | Q | f _n | K | Q | f _n | K | Q | f _n | K | Q | f _n |
| 2 | 1.586 | 0.707 | 1.000 | 1.268 | 0.577 | 1.273 | 1.842 | 0.864 | 1.231 | 2.114 | 1.129 | 0.907 |
| 4 | 1.152 2.235 | 0.541 1.307 | 1.000 1.000 | 1.034 1.759 | 0.522 0.806 | 1.432 1.606 | 1.582 2.660 | 0.705 2.941 | 0.597 1.031 | 1.924 2.782 | 0.929 4.587 | 0.471 0.964 |
| 6 | 1.068 1.586 2.483 | 0.518 0.707 1.934 | 1.000 1.000 1.000 | 1.040 1.364 2.023 | 0.510 0.611 1.024 | 1.607 1.692 1.908 | 1.537 2.448 6.494 | 0.684 1.812 6.494 | 0.396 0.768 1.011 | 1.891 2.648 2.904 | 0.902 2.841 10.417 | 0.316 0.730 0.983 |
| 8 | 1.038 1.337 1.889 2.610 | 0.510 0.601 0.900 2.564 | 1.000 1.000 1.000 1.000 | 1.024 1.213 1.588 2.184 | 0.506 0.560 0.711 1.225 | 1.781 1.835 1.956 2.192 | 1.522 2.379 2.711 2.913 | 0.677 1.610 3.460 11.494 | 0.297 0.599 0.861 1.006 | 1.879 2.605 2.821 2.946 | 0.892 2.532 5.587 18.519 | 0.238 0.572 0.842 0.990 |

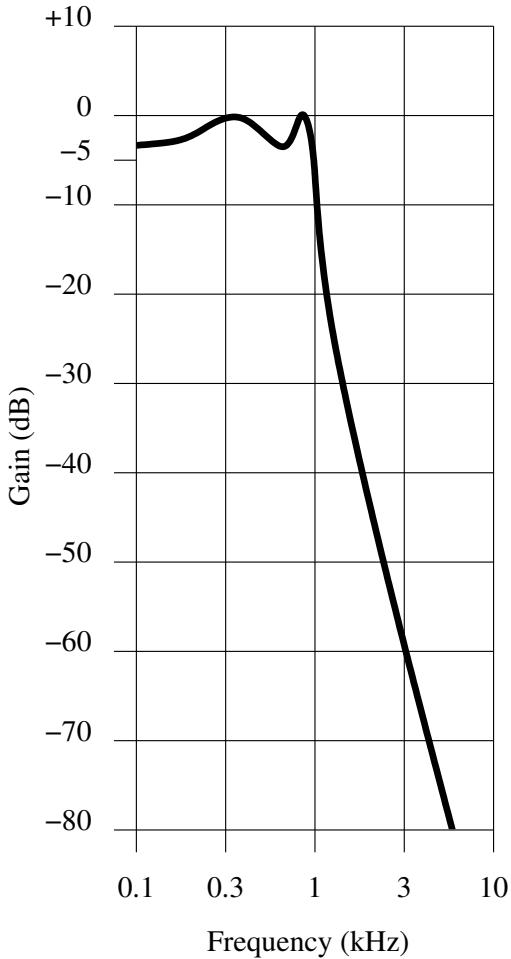1. (*?? points*) Based on the gain plotted below,
- (a) Is this filter high pass or low pass?
 - (b) What is the gain at DC?
 - (c) What is the critical frequency, f_c ?
 - (d) What is the roll-off (dB per decade) at high frequency?
 - (e) What is the passband ripple (dB)?
 - (f) What is the order (number of poles)?
 - (g) Butterworth, Bessel, or Chebyshev? How can you tell?




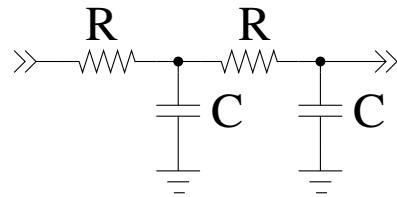


2. (*?? points*) Consider this simple 2-pole RC filter.

- (a) Calculate the complex response, $\frac{v_{\text{out}}}{v_{\text{in}}}$.
- (b) What are Q and ω_0 ?
- (c) What is the roll-off (how many dB per decade of frequency)?
Sketch gain (dB) vs. $\log \frac{\omega}{\omega_0}$.
- (d) *Qualitatively*, how would this filter differ from a 2-pole Butterworth in terms of (i) sharpness of the knee; (ii) time delay vs. frequency?

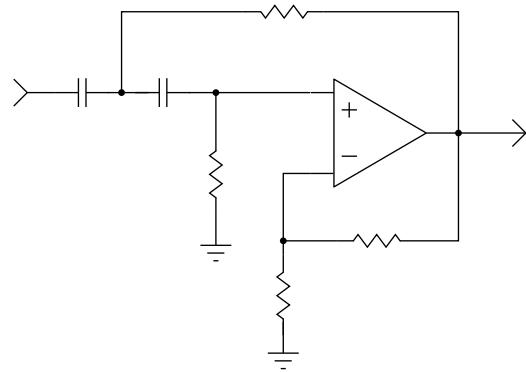
3. (*?? points*) For a generic 2-pole filter (high pass or low pass, your choice), work out the time delay in terms of ω , ω_0 , Q , and k .



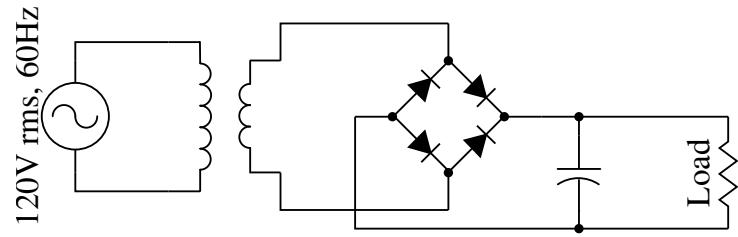4. (*?? points*) Choose resistor and capacitor values for the above circuit to make it a high-pass Butterworth filter. Specify values in terms of a desired critical frequency f_c .



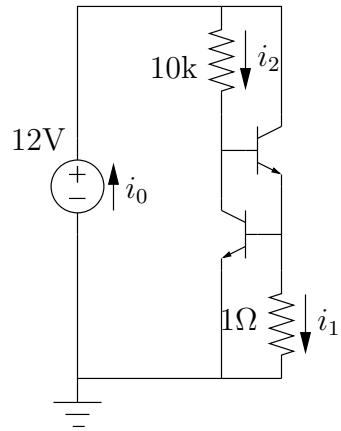5. (*?? points*) Choose a turn ratio for the transformer that gives 6 V peak output voltage (that is, 6 V amplitude). Assume 0.6 V per diode.
6. (*?? points*) Choose the capacitor value so that the output ripple is 1 mV across a 10Ω load.



7. (*?? points*) Assume 0.7V drop from base to emitter on both transistors.

- (a) Find the currents i_1 and i_2 .
- (b) Explain why $i_0 \leq i_1 + i_2$.
- (c) As an approximation, assume $i_0 = i_1 + i_2$. How much will i_0 change if the power supply voltage is doubled?

8. (*?? points*) The AC voltage

$$V(t) = V_0 \cos(2\pi t/T)$$

is attached to a resistor R . V_0 is called the amplitude.

- (a) What is the peak-to-peak voltage, V_{pp} ?
- (b) What is the root mean square voltage, V_{RMS} ?
- (c) How much power is dissipated in the resistor?
- (d) Inexpensive meters do not really measure V_{RMS} . It is easier to measure the *average absolute value*,

$$V_{AV} = \overline{|V(t)|} = \frac{1}{T} \int_0^T |V(t)| dt.$$

Calculate V_{AV} in terms of V_0 .

- (e) Given a circuit that measures V_{AV} , how would you scale that result to estimate V_{RMS} ?