

WE HAVE COVERED A SIGNIFICANT AMOUNT OF MATERIAL IN  
13 LECTURES ON DC AND AC CIRCUITS:

- OHM'S AND KIRCHHOFF'S LAWS
- CIRCUIT ANALYSIS TECHNIQUES
- DIODES & TRANSISTORS
- OPERATIONAL AMPLIFIERS
- NEGATIVE AND POSITIVE FEEDBACK  
(AMPLIFIERS, COMPARATORS, SCHMITT TRIGGERS)
- COMPLEX NUMBERS, PHASE, AND ALTERNATING CURRENT
- CAPACITORS, INDUCTORS, AND IMPEDANCE
- ANALYSIS OF SIMPLE AC CIRCUITS (GAIN AND PHASE)

TODAY, WE'LL FINISH BY DISCUSSING TRANSIENT ANALYSIS (CH.12)

- RC CIRCUITS
- LR CIRCUITS


# RC CIRCUITS

(2)

## DISCHARGING A CAPACITOR

SUPPOSE THE CAPACITOR IS

INITIALLY CHARGED TO VOLTAGE

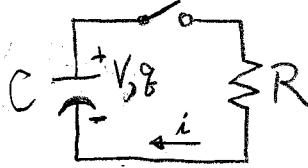

$V_0$ . AT TIME  $t=0$ , THE SWITCH IS CLOSED ( $\rightarrow$ ),  
COMPLETING THE CIRCUIT. FIND  $q(t)$ ,  $V(t)$ , AND  $i(t)$ .

THE CAPACITOR IS GOVERNED BY ITS DEFINING EQUATION,

$$q = CV.$$

NOW, APPLY KVL:

$$\frac{V}{C} - iR = 0 \quad (1)$$

BUT  $q$  AND  $i$  ARE JUST DIFFERENT WAYS OF KEEPING TRACK  
OF THE SAME THING:

$$i = \frac{-dq}{dt}. \quad (\text{WHY MINUS? LOOK AT THE CIRCUIT DIAGRAM})$$

SO EQUATION (1) BECOMES:

$$\frac{q}{C} + R \frac{dq}{dt} = 0$$

THIS IS A DIFFERENTIAL EQUATION, BUT A PARTICULARLY EASY ONE:

$$\frac{dq}{dt} = -\frac{q}{RC} \Rightarrow \int \frac{dq}{q} = \int -\frac{dt}{RC}$$


$$\Rightarrow \ln q = -\frac{t}{RC} + a$$

$$q(t) = e^{(-t/RC + a)} = e^a e^{-t/RC} = A e^{-t/RC}$$

Q: HOW DO WE FIND THE ARBITRARY CONSTANT,  $A$ ?

A: AT  $t=0$ ,  $V=V_0$ , SO  $q(0)=CV_0=A$ .
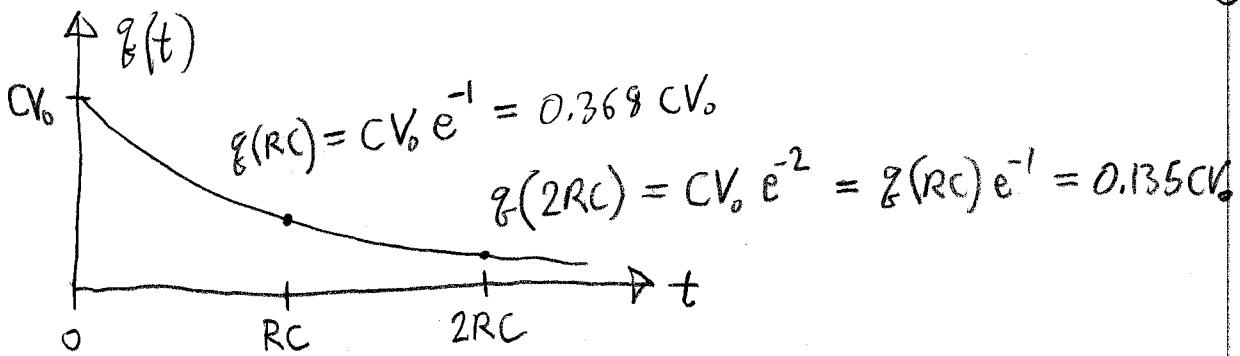
$$\therefore \boxed{q(t) = CV_0 e^{-t/RC}} \Rightarrow \begin{cases} q(0) = CV_0 \\ q(\infty) = 0 \end{cases} \left. \begin{array}{l} \text{MAKES} \\ \text{SENSE!} \end{array} \right\}$$



HOW ABOUT  $V(t)$ ?


$$V = \frac{q}{C}, \text{ so } V = V_0 e^{-t/RC} \quad - \text{ SAME BEHAVIOR AS THE CHARGE,}$$

AND NOW THE CURRENT; RECALL

$$\begin{aligned} i(t) &= -\frac{dq}{dt} \\ &= -CV_0 \left(\frac{-1}{RC}\right) e^{-t/RC} \end{aligned}$$

$i(t) = \frac{V_0}{R} e^{-t/RC}$

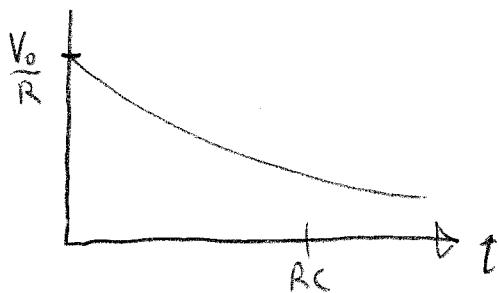so  $i(0) = \frac{V_0}{R}$  ✓ MAKES SENSE!




NOTE THE DIMENSIONLESS VARIABLES:

$$t \rightarrow t/RC, \quad V \rightarrow V/V_0, \quad q \rightarrow q/CV_0, \quad i \rightarrow iR/V_0$$

$$\frac{V}{V_0} = \frac{q}{CV_0} = \frac{iR}{V_0} = e^{-t/RC}$$
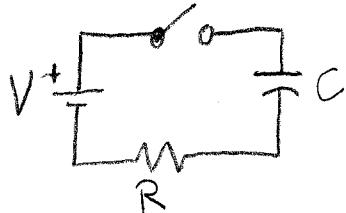
## CHARGING A CAPACITOR

SUPPOSE THE CAPACITOR IS INITIALLY UNCHARGED ( $q = 0$ ). CLOSE THE SWITCH AT TIME  $t = 0$ .



SWITCHES:



CLOSED

$$\text{RECALL: } q = CV$$

$$\text{KVL: } V - \frac{q}{C} - iR = 0 \quad (2)$$

$$\text{Now, } i = \frac{dq}{dt} \quad (\text{WHY PLUS?})$$

SO OUR EQUATION (2) BECOMES

$$CV - q - RC \frac{dq}{dt} = 0 \quad (3)$$

SUPPOSE WE TRY SOMETHING LIKE THE SOLUTION TO THE LAST PROBLEM:

$$q = Ae^{-t/RC}$$

PLUG INTO (3):

$$CV - Ae^{-t/RC} + Ae^{-t/RC} = 0$$

$$CV = 0 ?!$$

WHAT MIGHT WE DO TO FIX UP THE SOLUTION?


PHYSICALLY, AS  $t \rightarrow \infty$ , WE SHOULD HAVE

$$\lim_{t \rightarrow \infty} q(t) \rightarrow CV \quad (\text{WHY?})$$


TRY  $q(t) = Ae^{-t/RC} + CV$  ✓ THIS SATISFIES (3).

NOW, WE WANT  $q(0) = 0$ , SO  $A = -CV$ .

$$\therefore q(t) = CV(e^{-t/RC} - 1)$$

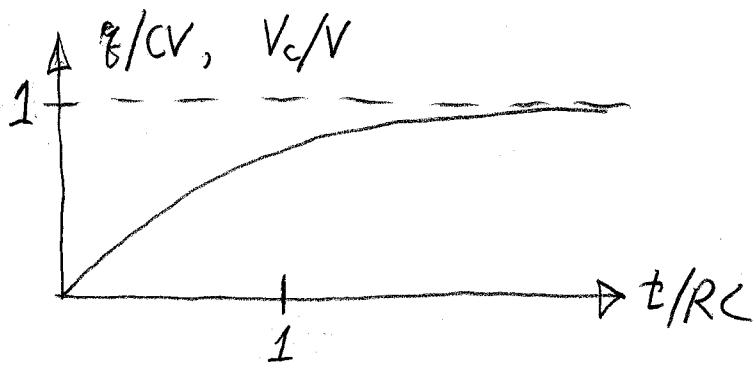

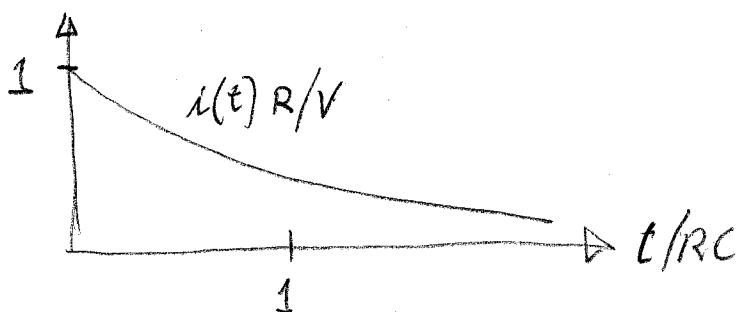BUT  $i(t) = \frac{V}{R} e^{-t/RC}$  ( $\frac{iR}{V} = e^{-t/RC}$ )



### GENERAL CONCEPT FOR TRANSIENT ANALYSIS:

GIVEN A TIME-VARYING QUANTITY  $X(t)$  (PERHAPS  $i, q, V$ ),

- ① FIGURE OUT THE INITIAL VALUE,

$$X(0) = X_0$$

- ② FIGURE OUT THE FINAL VALUE,

$$\lim_{t \rightarrow \infty} X(t) = X_\infty$$

- ③ FIND THE RELEVANT TIME CONSTANT,  $\tau$

(FOR RC CIRCUITS,  $\tau = RC$ )

- ④ THE SOLUTION IS:


$$X(t) = [X_0 - X_\infty] e^{-t/\tau} + X_\infty$$

} WORKS FOR  
RC OR LR.  
LC OR LRC  
CAN OSCILLATE.

- ⑤ USE KVL TO FIND THE DIFFERENTIAL EQUATION.  
PLUG IN AND CHECK YOUR SOLUTION.

# RL CIRCUITS

6

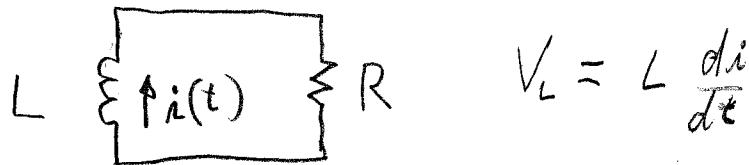

$$V_L = L \frac{di}{dt}$$


$$\text{KVL: } -L \frac{di}{dt} - iR = 0$$

$$\frac{di}{dt} = -\frac{R}{L} i \Rightarrow i = A e^{-tR/L}$$

SO, THE TIME CONSTANT FOR AN RL CIRCUIT IS

$$\tau = \frac{L}{R}$$

EXAMPLE

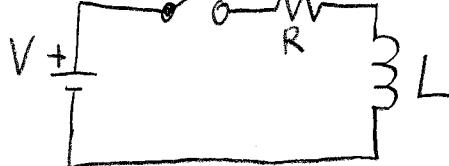

SWITCH IS CLOSED AT  $t=0$ .  
FIND  $i(t)$ .

$$\textcircled{1} \quad i(0) = 0$$

$$\textcircled{2} \quad i(\infty) = V/R \quad (\text{DISCUSS?})$$

$$\textcircled{3} \quad \tau = L/R$$

$$\textcircled{4} \quad i(t) = \left[0 - \frac{V}{R}\right] e^{-Rt/L} + \frac{V}{R} = \frac{V}{R} \left(1 - e^{-Rt/L}\right)$$

$$\textcircled{5} \quad \text{KVL: } V - iR - L \frac{di}{dt} = 0; \quad \text{PLUG IN MY SOLUTION:}$$

$$V - V \left(1 - e^{-Rt/L}\right) - \cancel{\left(\frac{-V}{R}\right)} \cancel{\left(\frac{-R}{L}\right)} e^{-Rt/L} = 0?$$

$$+ V e^{-Rt/L} - V e^{-Rt/L} = 0 \quad \checkmark$$

Q: WHAT ABOUT THE VOLTAGE ACROSS THE INDUCTOR,  $V_L(t)$ ?

A:

$$V_L = L \frac{di}{dt} = \frac{LV}{R} \cdot \frac{R}{L} \cdot e^{-Rt/L} = V e^{-Rt/L}$$

EXERCISE: TRY DERIVING  $V_L(t)$  FROM SCRATCH USING THE 5-STEP PROCESS.