

Physics 261

Exam 1


70 points possible.

Remember to show your work.

Name: Solution

12:00 - 12:10

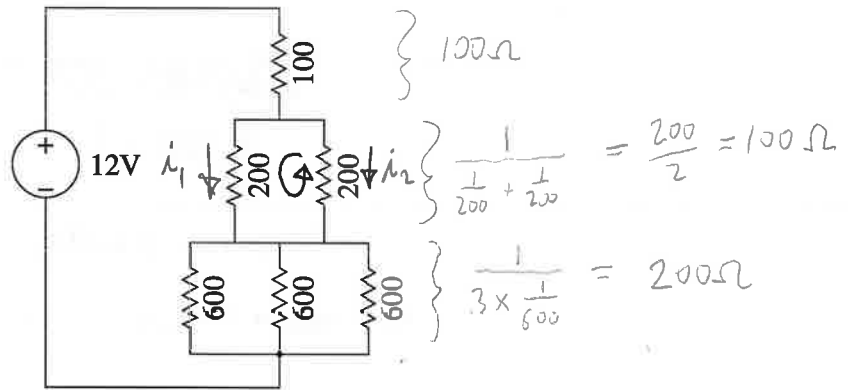1. Six resistors are attached to a power supply, as shown.



- (a) (5 points) Find the equivalent resistance.
 (b) (5 points) How much power is dissipated in this circuit?
 (c) (5 points) Use Kirchhoff's Voltage Law to show that the two 200Ω resistors must have equal current.


(a) $100 + 100 + 200 = \boxed{400\Omega}$

(b) $P = IV; I = \frac{12V}{400\Omega} = 0.03A = \boxed{30mA}$
 $P = 30mA \times 12V = \boxed{360mW}$ or $\frac{144}{400}W$

(c) KVL: $i_1(200\Omega) - i_2(200\Omega) = 0$

$\Rightarrow i_1 - i_2 = 0 \Rightarrow i_1 = i_2$

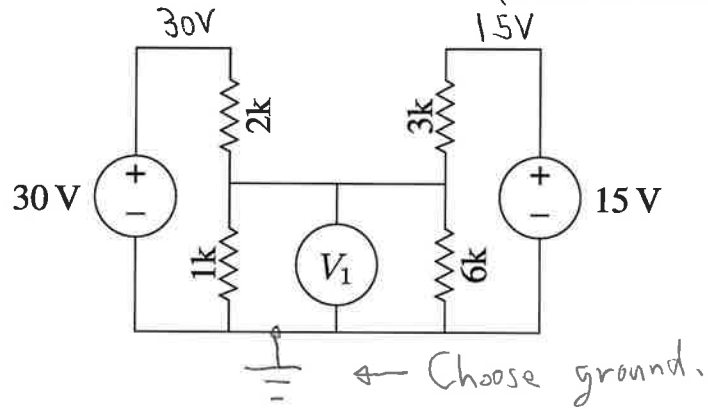2. (20 points) Use Node Voltage Analysis to find the voltage measured by the meter, V_1 . Assume that the meter is ideal (draws no current).



KCL:

$$\frac{30V - V_1}{2k\Omega} + \frac{0 - V_1}{1k\Omega} + \frac{15V - V_1}{3k\Omega} + \frac{0 - V_1}{6k\Omega} = 0$$

Multiplying by $6k\Omega$ and collecting terms,

$$90V + 30V - V_1(3 + 6 + 2 + 1) = 0$$

$$V_1 = \frac{120V}{12} = \boxed{10V}$$

+5

$$+3 \times 4 = 12$$

+3


-3 for no NVA
but correct

12:16-12:19

3. In the real world, batteries are not ideal voltage sources. A Thévenin or Norton equivalent is a better (though still not perfect) model. Suppose a button cell battery has an output voltage of 1.5 V when connected directly to a voltmeter. It delivers 100 mA when connected directly to an ammeter.

(a) (10 points) Sketch the Thévenin equivalent of the battery and give values for V_{Th} and R_{Th} .

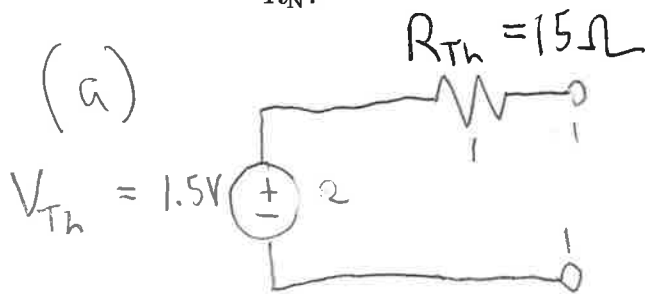(b) (5 points) Also sketch the Norton equivalent. What are I_N and R_N ?




$$I_{oc} = 100 \text{ mA}$$

$$R_{Th} = \frac{V_{Th}}{I_{oc}} = \frac{1.5 \text{ V}}{100 \text{ mA}} = 15 \Omega$$

(b)
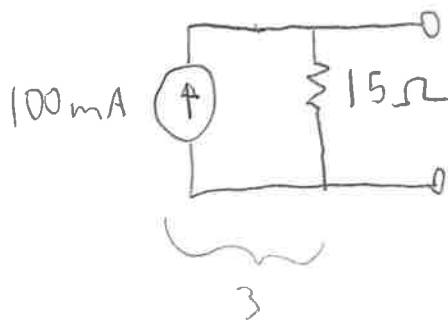
$$\left. \begin{aligned} I_N &= I_{oc} = 100 \text{ mA} \\ R_N &= R_{Th} = 15 \Omega \end{aligned} \right\}$$




12:20 - 12:28

4. Sketch a Wheatstone Bridge similar to the one we used in class. A thin wire, laid along a meter stick, is the potentiometer along one side of the bridge. Assume the wire's total resistance is $10\ \Omega$. Connected at 0 mm is $R_{\text{ref}} = 11\ \Omega$. Connected to the reference and also to the wire at 1000 mm, is $R_{\text{test}} = 99\ \Omega$. A galvanometer connects these two resistors to the potentiometer wiper.

(a) (5 points) At what position along the meter stick must the wiper be set to zero the galvanometer?

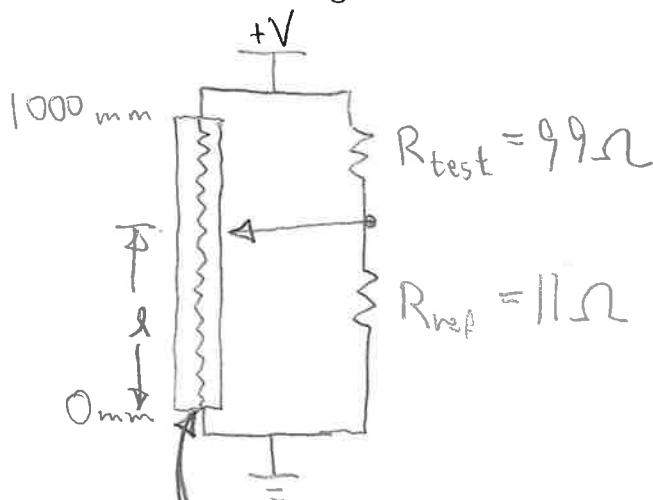(b) (10 points) Unfortunately, the wire just broke somewhere between the 0 mm and 1 mm mark. You try to repair it, but there's an extra $1\ \Omega$ of resistance at the repair. Now where must the wiper be set to zero the galvanometer?



$$(a) \frac{l}{1000\text{ mm}} = \frac{11\ \Omega}{99\ \Omega + 11\ \Omega}$$

$$l = 1000 \left(\frac{11}{110} \right) = 100\text{ mm}$$

(b) $+1\ \Omega$ (oops!)

$$\frac{(l/1000\text{ mm}) 10\ \Omega + 1\ \Omega}{10\ \Omega + 1\ \Omega} = \frac{11\ \Omega}{99 + 11\ \Omega} = \frac{1}{10}$$

$$\frac{l}{1000\text{ mm}} 10\ \Omega + 1\ \Omega = \frac{11\ \Omega}{10} = 1.1\ \Omega$$

5

$$l = 1000\text{ mm} \left(\frac{1.1\ \Omega - 1\ \Omega}{10\ \Omega} \right) = \frac{1000\text{ mm}}{10} = 10\text{ mm}$$