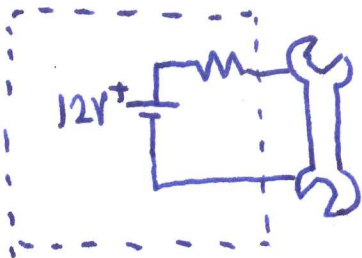


1. A mechanic drops a wrench across both terminals of a 12 V motorcycle battery. This puts 120 A through the wrench. Assume all the resistance is inside the motorcycle battery ($R = 0$ for the wrench.)

- (a) (4 points) What is the total resistance of the circuit?
 (b) (4 points) How much power is dissipated? ~~4~~ I MEANT TOTAL. THIS WAS CLARIFIED IN THE AFTERNOON.
 (c) (3 points) What is the voltage across the wrench?
 (d) (6 points) Find and draw Thevenin and Norton equivalents for the battery (without the wrench).

MOTORCYCLE
BATTERY



(a) $V = IR$


$R = 12V / 120A = 0.1 \Omega$

(b) $P = IV = 12V \cdot 120A = 1440 W$


(c) SINCE THE WRENCH HAS $R = 0$, $\Delta V = 0$.

(d) $V_{oc} = 12V$
 $I_{sc} = 120A$ } $\Rightarrow R_{TH} = 0.1 \Omega$


THEVENIN:

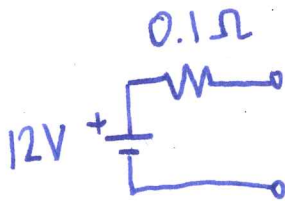

NORTON:

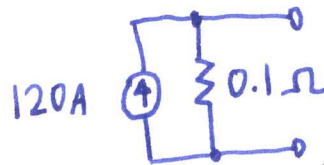

2. Consider the following circuit.

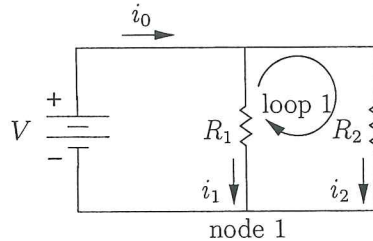

- (a) (4 points) Write KVL for loop 1.
- (b) (4 points) Write KCL for node 1.
- (c) (4 points) Combine the above to eliminate i_2 and solve for i_1 .¹

$$(a) \quad -i_1 R_1 + i_2 R_2 = 0$$

$$(b) \quad i_0 = i_1 + i_2$$

$$(c) \quad i_2 = i_0 - i_1 ; \text{ SUBSTITUTE THIS INTO (a):}$$


$$-i_1 R_1 + (i_0 - i_1) R_2 = 0$$

$$\Rightarrow i_0 R_2 = i_1 (R_1 + R_2)$$

$$\therefore i_1 = \left(\frac{R_2}{R_1 + R_2} \right) i_0$$

$$\text{OR EQUIVALENTLY: } i_1 = \left(\frac{G_1}{G_1 + G_2} \right) i_0.$$

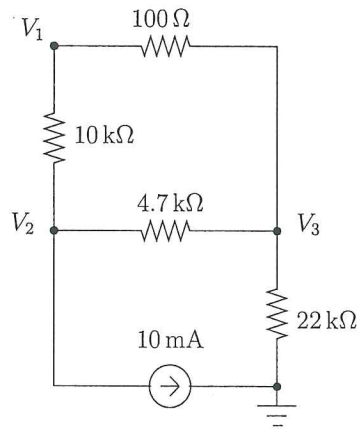¹The result should be the familiar current divider formula.



3. (11 points) Set up, but do not solve, the equations for node voltage analysis of this circuit. The only unknowns should be V_1 , V_2 and V_3 .

$$\text{NODE 1: } \frac{V_3 - V_1}{100} + \frac{V_2 - V_1}{10k} = 0$$


$$\text{NODE 2: } \frac{V_1 - V_2}{10k} + \frac{V_3 - V_2}{4.7k} - 10 \text{ mA} = 0$$

$$\text{NODE 3: } \frac{V_2 - V_3}{4.7k} + \frac{V_1 - V_3}{100} + \frac{0 - V_3}{22k} = 0$$

ALTERNATIVELY, FOR NODE 3 WE COULD GET THE VOLTAGE DIRECTLY:

$$V_3 = (22k\Omega)(-10 \text{ mA}) = -220 \text{ V.}$$

4. (10 points) Find R_1 and R_2 .

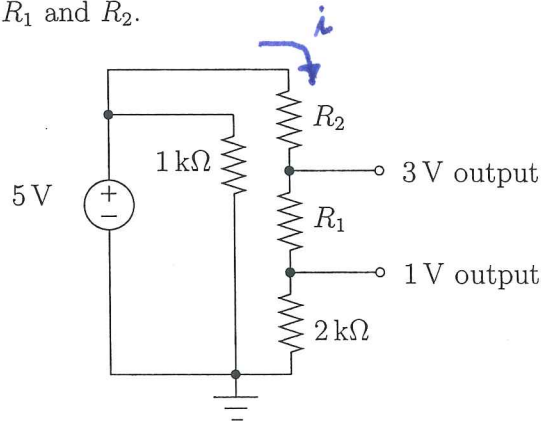

NOTE THAT THE $1k\Omega$ RESISTOR IS IRRELEVANT!

METHOD 1: $1V = i \cdot 2k\Omega \Rightarrow i = \frac{1}{2} \text{ mA}$
 $3V = 1V + iR_1 \Rightarrow R_1 = \frac{2V}{i} = \underline{4k\Omega}$
 $5V = 3V + iR_2 \Rightarrow R_2 = \frac{2V}{i} = \underline{4k\Omega}$

COULD ALSO USE VOLTAGE DIVIDER FORMULA:

METHOD 2: $V_{OUT} = \left(\frac{R_{BOTTOM}}{R_{TOTAL}} \right) V_{TOP}$

SO $1V = \left(\frac{2k\Omega}{R_1 + 2k\Omega} \right) 3V \Rightarrow R_1 = \underline{4k\Omega}$

$3V = \left(\frac{R_1 + 2k\Omega}{R_1 + R_2 + 2k\Omega} \right) 5V = \left(\frac{6k\Omega}{R_2 + 6k\Omega} \right) 5V$
 $\Rightarrow R_2 = \underline{4k\Omega}$

