

OUTLINE

LAST TIME: (CH. 5)

COMPLEX NUMBERS

MAGNITUDE

COMPLEX CONJUGATE

EULER'S FORMULA

THIS TIME: (CH. 7)

ALTERNATING CURRENT

- SINE & COSINE, ω , f , T

- POWER

- PHASE SHIFT

- COMPLEX REPRESENTATION (PHASORS)

NEXT TIME: (CH. 8)

- CAPACITORS

- INDUCTORS

- COMPLEX IMPEDANCE

Before we get started on today's topic, Faissler provides the following trig identities (p. 59):

$$\sin^2 a + \cos^2 a = 1 \quad (7-15)$$

$$\sin(a + b) = \sin a \cos b + \cos a \sin b \quad (7-16)$$

$$\cos(a + b) = \cos a \cos b - \sin a \sin b \quad (7-17)$$

$$\sin 2a = 2 \sin a \cos a \quad (7-18)$$

$$\cos 2a = 2 \cos^2 a - 1 = 1 - 2 \sin^2 a \quad (7-19)$$

Faissler has some $\pm$ operators in his trig identities. These are not necessary if you consider a & b to be signed quantities. For example, (7-17) implies that

$$\cos(a - b) = \cos a \cos b + \sin a \sin b.$$

You will derive (7-16) and (7-17) for homework. Let's derive (7-18) and (7-19) as an example. Using Euler's formula,

$$e^{2ja} = \cos 2a + j \sin 2a.$$

Alternatively, we could write

$$e^{2ja} = (e^{ja})^2 = (\cos a + j \sin a)^2 = \cos^2 a - \sin^2 a + 2j \cos a \sin a.$$

Either way we go about expressing e^{2ja} , we get a complex result of course. The only way for the two results to match is if both the real *and* the imaginary parts match. That's how we get to (7-18) and (7-19). The later requires also employing (7-15), so that we can have our result in terms of just the cosine, or just the sine.

SO FAR, WE HAVE BEEN DEALING WITH "DIRECT CURRENT" (DC):

$$V = \text{CONSTANT } 5V \quad \text{---} \oplus \quad \text{---} \ominus \quad 3mA$$


$$i = \text{CONSTANT}$$

NOW CONSIDER "ALTERNATING CURRENT" (AC). EXAMPLES:

$$i(t) = i_0 \cos(\omega t)$$

OR $i(t) = i_0 \sin(\omega t)$

$$\text{---} \oplus \quad i(t)$$

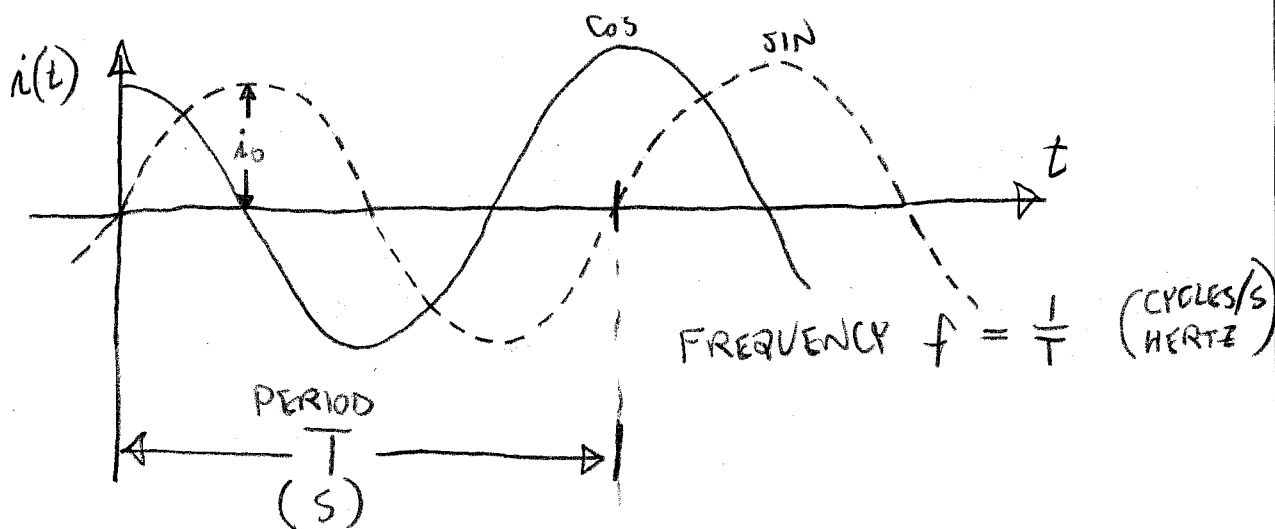

THE QUANTITY ω (RADIAN/SEC) IS CALLED THE "ANGULAR FREQUENCY". IT IS RELATED TO T & f AS FOLLOWS:


$$\omega T = 2\pi$$

$$\Rightarrow T = \frac{2\pi}{\omega} \quad \leftarrow \text{SECONDS, } s$$

$$\Rightarrow f = \frac{\omega}{2\pi} \quad \leftarrow \text{HERTZ, } Hz$$

WE MAY SIMILARLY HAVE


$$V(t) = V_0 \cos(\omega t)$$

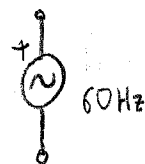

THIS IS STILL CALLED AC (ALTERNATING CURRENT), EVEN THOUGH IT IS VOLTAGE!

SUPPOSE

$$V = V_0 \cos(\omega t)$$

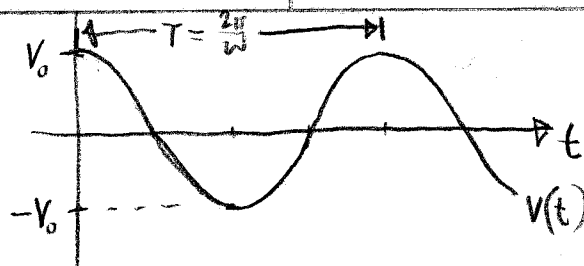


WHAT IS THE POWER DISSIPATED IN THE RESISTOR?

RECALL

$$P = iV; \quad i = \frac{V}{R} = \frac{V_0}{R} \cos(\omega t)$$

$$\therefore P = \frac{V_0^2}{R} \cos^2(\omega t)$$
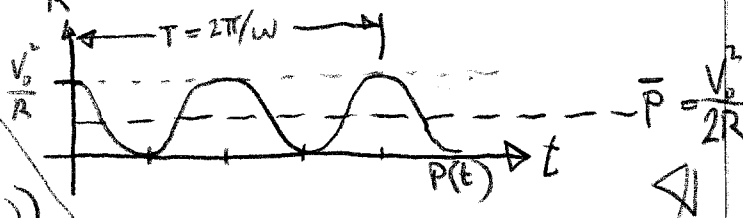
$$= \frac{V_0^2}{R} \frac{1}{2} (1 + \cos(2\omega t))$$



WHAT IS THE TIME AVERAGE OF THE POWER?

$$\bar{P} = \frac{1}{T} \int_0^T P dt = \frac{1}{T} \int_0^T \frac{V_0^2}{2R} (1 + \cos(2\omega t)) dt$$

$$\text{LET } \omega t = \theta, \quad dt = \frac{d\theta}{\omega}$$

$$\bar{P} = \frac{1}{T} \int_0^{2\pi} \frac{V_0^2}{2R\omega} (1 + \cos 2\theta) d\theta = \frac{\hat{V}_0^2}{2R\omega T} \left(\theta + \frac{1}{2} \sin 2\theta \right)_0^{2\pi}$$

$$= \frac{V_0^2}{2R\omega \left(\frac{2\pi}{\omega}\right)} 2\pi = \frac{1}{2} \frac{V_0^2}{R}$$

✓ COMPARE TO THE GRAPHICAL RESULT ABOVE


PHASE SHIFTS

$$V = V_0 \cos(\omega t + \phi)$$

$$= V_0 \cos(\omega[t + \Delta t]) ; \text{ so } \omega \Delta t = \phi$$

↑ TIME ADVANCE

STARTS AT
EARLIER

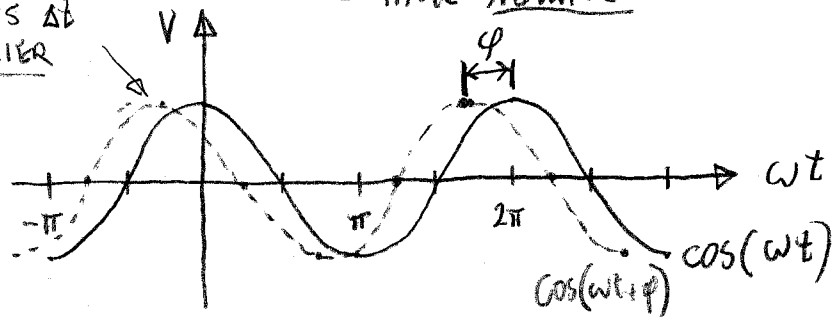



WHAT HAPPENS IF VOLTAGE & CURRENT ARE "OUT OF PHASE" ?

i.e. $V = V_0 \cos(\omega t)$

$$i = i_0 \cos(\omega t + \phi)$$

} DIFFERENT PHASE!

FOR EXAMPLE, $\phi = \frac{\pi}{2}$:

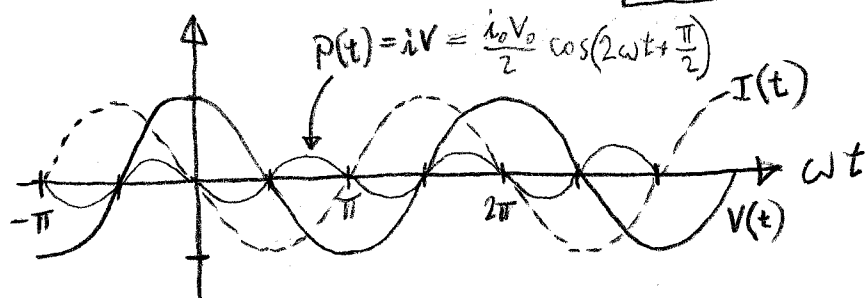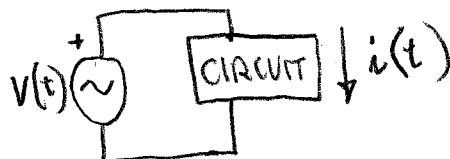

$P > 0$: CIRCUIT IS DISSIPATING POWER

$P < 0$: CIRCUIT IS A POWER SOURCE
(SENDING POWER BACK INTO THE
VOLTAGE SOURCE)

Q: FOR $\phi = \frac{\pi}{2}$, WHAT IS $\bar{P}$?

A: $\bar{P} = 0$. THERE IS NO AVERAGE POWER, BECAUSE THE POSITIVE
PEAKS AND NEGATIVE VALLEYS EXACTLY CANCEL.

MORE GENERALLY,

$$i = i_0 \cos(\omega t + \phi)$$

$$v = v_0 \cos(\omega t)$$

THEN

$$p = i v = i_0 v_0 (\cos \omega t \cos \phi - \sin \omega t \sin \phi) \cos \omega t$$

$$= i_0 v_0 \left(\underbrace{\cos^2 \omega t}_{\frac{1}{2}(1 + \cos 2\omega t)} \cos \phi - \underbrace{\sin \omega t \cos \omega t}_{\frac{1}{2} \sin 2\omega t} \sin \phi \right)$$

$$= \frac{i_0 v_0}{2} \left[(1 + \cos 2\omega t) \cos \phi - \sin 2\omega t \sin \phi \right]$$

$$= \frac{i_0 v_0}{2} \left[\cos \phi + \underbrace{\cos 2\omega t \cos \phi - \sin 2\omega t \sin \phi}_{\cos(2\omega t + \phi)} \right]$$

$$= \frac{i_0 v_0}{2} \left[\cos \phi + \cos(2\omega t + \phi) \right]$$

AMPLITUDE

MEAN
VALUE

TIME VARIATION
WITH MEAN OF ZERO

SIMILARLY, IF

$$i = i_0 \cos(\omega t + \phi_1), \text{ AND}$$

$$v = v_0 \cos(\omega t + \phi_2), \text{ THEN}$$

$$p = i v = \frac{i_0 v_0}{2} \left[\cos(\phi_2 - \phi_1) + \cos(2\omega t + \phi_1 + \phi_2) \right]$$

$$\underline{\underline{\bar{p} = \frac{i_0 v_0}{2} \cos(\phi_2 - \phi_1)}}$$

USING COMPLEX NUMBERS TO REPRESENT AC:

IF $V = V_0 \cos(\omega t + \phi)$, WE WRITE

$$\tilde{V} = V_0 e^{j(\omega t + \phi)} = \tilde{V}_0 e^{j\omega t}$$

$|\tilde{V}|$ = AMPLITUDE

↑
ANGULAR
FREQUENCY


↑
COMPLEX
AMPLITUDE

↑
PHASE SHIFT

$$\tilde{V}_0 = V_0 e^{j\phi}$$

THE COMPLEX AMPLITUDE
ENCODS THE PHASE SHIFT,
AS WELL AS THE AMPLITUDE.

GRAPHICALLY:

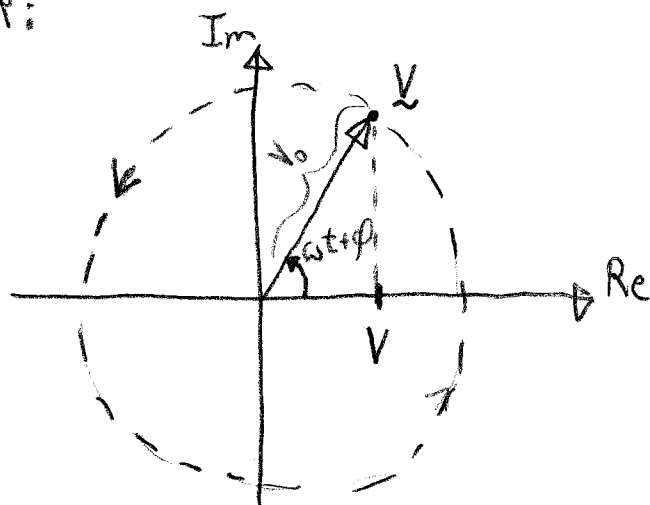

THE "PHASOR" (ARROW)
HOLDS CONSTANT RADIUS
 V_0 AS IT ROTATES
COUNTER CLOCKWISE.


RECALL THAT IN OUR STUDY OF POWER, WE FOUND

IF $i = i_0 \cos(\omega t + \phi_1)$, $V = V_0 \cos(\omega t + \phi_2)$, THEN

$$\bar{P} = \frac{1}{2} i_0 V_0 \cos(\phi_2 - \phi_1) = \frac{1}{2} i_0 V_0 \cos(\phi_1 - \phi_2)$$

THIS IS LIKE A
DOT PRODUCT,
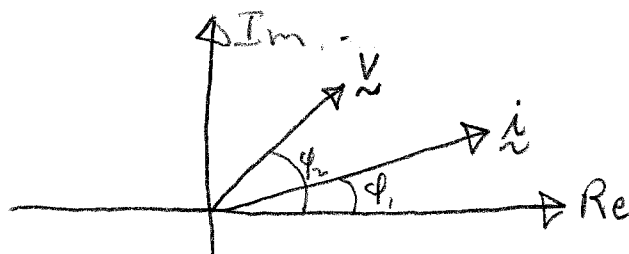
$$\underline{\tilde{i}} \cdot \underline{\tilde{V}}$$



CONSIDER: $\underline{\tilde{z}} \cdot \underline{\tilde{z}} = |\underline{\tilde{z}}|^2 \equiv \underline{\tilde{z}}^* \underline{\tilde{z}}$

$$\begin{aligned} \text{BY ANALOGY, TRY } \bar{P} &= \frac{1}{2} \underline{\tilde{i}} \cdot \underline{\tilde{V}} = \frac{1}{2} \underline{\tilde{i}}^* \underline{\tilde{V}} = \frac{1}{2} i_0 e^{-j(\omega t + \phi_1)} V_0 e^{j(\omega t + \phi_2)} \\ &= \frac{1}{2} i_0 V_0 e^{j(\phi_2 - \phi_1)} \end{aligned}$$

Q: IS THIS RIGHT?

A: ALMOST.

$$\boxed{\bar{P} = \frac{1}{2} \operatorname{Re}(i^* v) = \frac{1}{2} \operatorname{Re}(i v^*)}$$

$$= \frac{1}{2} i_0 V_0 \cos(\phi_2 - \phi_1) = \frac{1}{2} i_0 V_0 \cos(\phi_1 - \phi_2)$$

TO SEE HOW THIS "DOT" PRODUCT WORKS, CONSIDER THE ORDINARY DOT PRODUCT:

$$\begin{bmatrix} a \\ b \end{bmatrix} \cdot \begin{bmatrix} c \\ d \end{bmatrix} = ac + bd$$

IN THE COMPLEX PLANE,

$$(a + jb) \cdot (c + jd) \equiv \operatorname{Re}[(a + jb)^*(c + jd)]$$

$$= \operatorname{Re}[(a - jb)(c + jd)] =$$

$$= \operatorname{Re}[ac + bd + j(ad - bc)]$$

$$= \boxed{ac + bd} \checkmark$$

INTERESTINGLY, THE IMAGINARY PIECE
IS THE CROSS PRODUCT!